

Designing with UnitedSiC FETs

Pete Losee

Manager Device Technology Development

December 2018

Contents

- Introduction to the UnitedSiC FET portfolio
- General Gate Drive Guidelines
- Using snubbers to manage switching waveforms
- Benefits of packages with Kelvin connections
- UnitedSiC FET User Guide
- Tips for paralleling TO packages

SiC Application Growth



Server & Datacenter



Lighting & Electronic Ballast



Electric Vehicles



Lab & Din Rail PSU



Battery Charging



Renewable Energy & Storage

Key Features



UJ3C & UF3C Series, 650/1200V SiC FETs


Key Features

- Excellent body diode performance ($V_f < 2V$)
- Drive with any Si and/or SiC gate drive voltage
- High performance cascode configuration
- Superior thermal performance
- Integrated ESD and gate protection
- Kelvin package (UF3C Fast series)

Drop-in Functionality Without Changing Gate Drive Voltage


(Replaces Si IGBTs, Si FETs, SiC MOSFETs or Si Superjunction Devices)

12V/0V Operation Simplifies Upgrading

 

Innovative cascode configuration enables Si and SiC gate voltage compatibility


Superior Gate and ESD Protection

 


Integrated clamping diode protects gates from $|25V|$ and adds ESD protection




UnitedSiC Product Portfolio

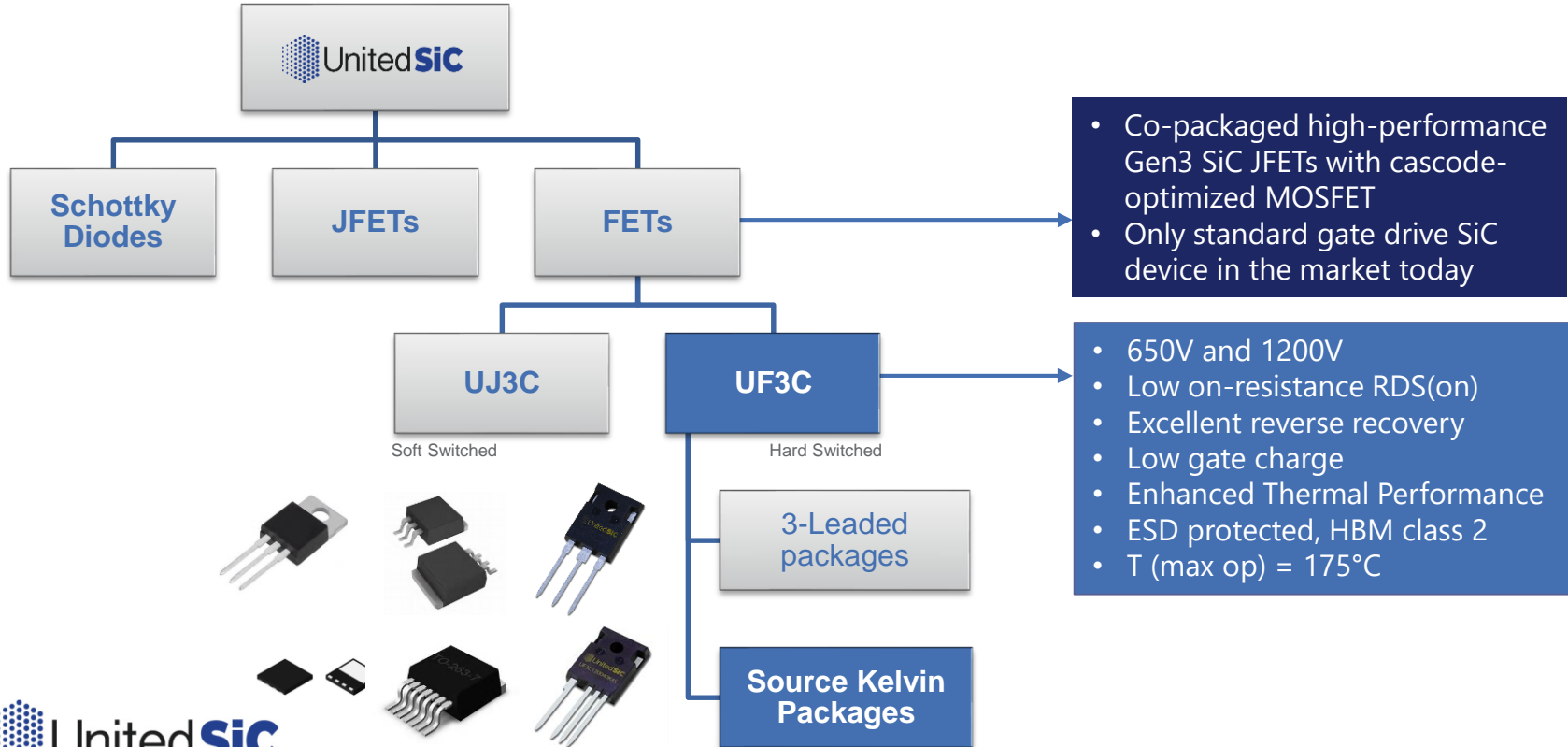


UF3C performance benefits

1200V Devices	UJ3C120040K3S	UF3C120040K3S
Qrr (150°C)	482nC	289nC 
Rds(on)	35mohm	35mohm
VF(20A)	1.5V	1.5V

650V Devices	UJ3C065030K3S	UF3C065030K3S
Qrr (150°C)	400nC	188nC 
Rds(on)	27mohm	27mohm
VF(20A)	1.3V	1.3V

- Lower losses for higher frequency switching circuits, especially where hard switching at turn-on is needed
- No changes to thermal resistance or current ratings

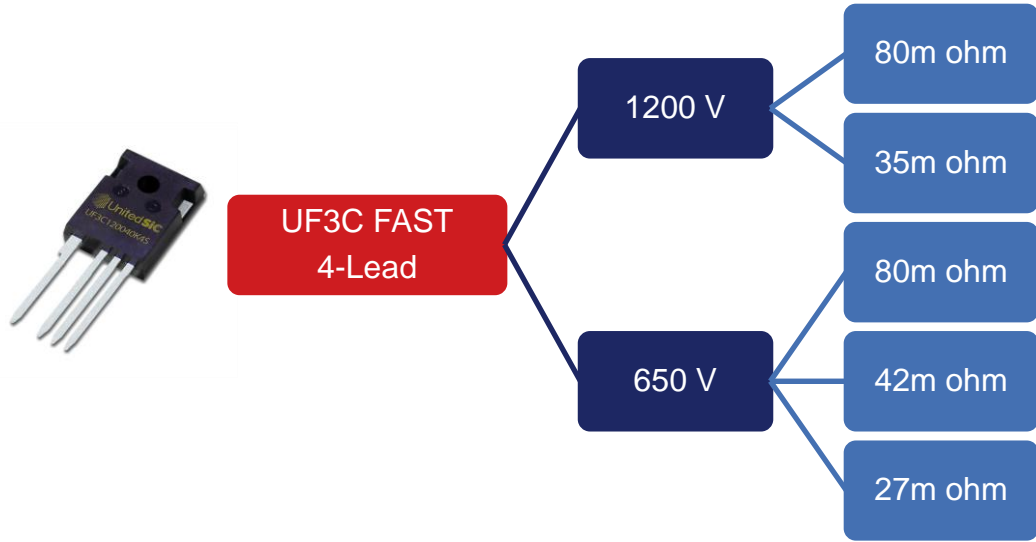UF3C FAST SiC FETs in 4-lead kelvin connected package



All the benefits of UnitedSiC
SiC FETs

PLUS


- *Extremely fast switching*
- *Lowest switching losses*
- *Clean gate waveforms*
- *No false triggering*

Turn-off Waveforms

UF3C120040K3S




UF3C120040K4S

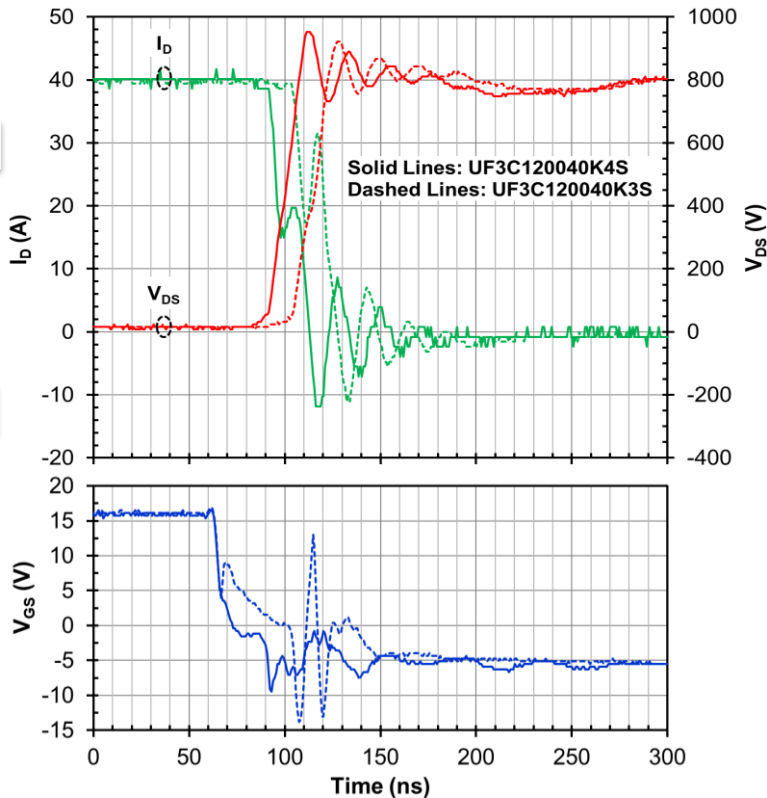

- UF3C120040K3S: $E_{off} = 208\mu J$
- UF3C120040K4S: $E_{off} = 170\mu J$

Turn-on Waveforms

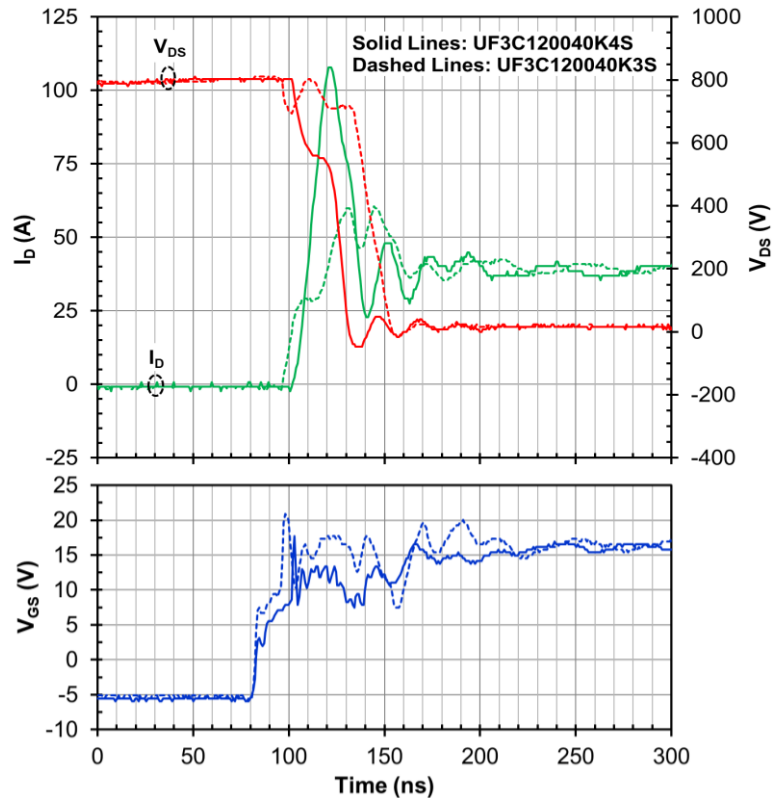

- UF3C120040K3S: $E_{on} = 1300\mu J$, $di/dt = 3800A/\mu s$
- UF3C120040K4S: $E_{on} = 845\mu J$, $di/dt = 7100A/\mu s$



800V, 40A, Half-bridge, RT, $R_{gon} = 3\Omega$, $R_{goff} = 10\Omega$, FWD: $V_{gs} = -5V$, $R_g = 10\Omega$; $R_{SNUB} = 10\Omega$, $C_{SNUB} = 220pF$


General Gate Drive Guidelines

- UnitedSiC cascode FET $V_{th}=5V$
- $V_{gsmax} = +/-25V$
- Gate drive 0 to 12V is best, especially in ZVS applications
- No issues with negative gate drive. Any voltages $+/-20V$ may be used with the right R_g changes
- Devices are compatible with a wide range of gate drives and gate drive ICs – both Si MOS/IGBT drivers as well as newer SiC MOSFET drivers
- Also compatible with simple gate drive transformers

Drop-in Functionality Without Changing Gate Drive Voltage


(Replaces Si IGBTs, Si FETs, SiC MOSFETs or Si Superjunction Devices)

12V/0V Operation Simplifies Upgrading

 

Innovative cascode configuration enables Si and SiC gate voltage compatibility

Superior Gate and ESD Protection

 

Integrated clamping diode protects gates from $|25V|$ and adds ESD protection

Cascode switching and gate charge



 


Figure 8 Typical gate charge
at $V_{DS} = 800V$ and $I_D = 40A$

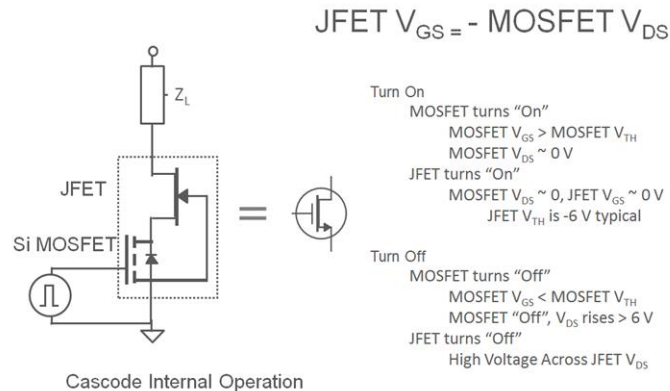

- Gate charge comes from the LVMOS
- Same LVMOS used across many products leads to same Q_g across many products
- Cascode dV/dt is controlled primarily by JFET built-in R_g (fixed) and secondarily by external MOSFET R_g (user controlled)
- Generally, turn-off is much faster than turn-on in cascodes, so it needs a higher R_{goff}

V_{GS} Effect on E_{SW} for TO247-3L

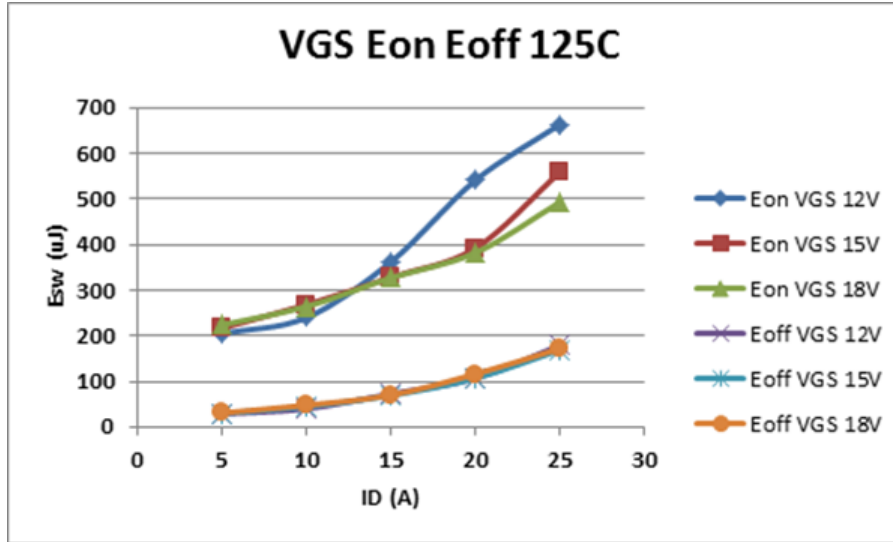

HALF BRIDGE
UJ3C120080KS
HS+LS


$R_{gon}=1\text{ohm}$
 $R_{goff}=20\text{ohm}$
Both HS and LS

$T_j=125\text{C}$

At higher currents, a $V_{gs}>12\text{V}$ allows faster turn-on for lower E_{on} .

Not much difference below 15A

 Comparison of Switching Losses with and without using Ferrite Bead




Part #: BLM41PG600SN1L
Description: FERRITE BEAD
60 OHM 1806 1LN

Looks like 100nH at 100MHz

3. Rating


Customer Part Number	MURATA Part Number	Impedance (Ω) (at 100MHz, Under Standard Testing Condition)		Rated Current (mA) (*1)		DC Resistance (Ω) max.		Remark
		Typical	at 85°C	at 125°C	Initial Values	Values After Testing		
	BLM41PG600SN1L	30 min.	60	*1	*1	0.009	0.018	For DC power line
	BLM41PG600SN1B			6000	3700			
	BLM41PG750SN1L	45 min.	75	*1	*1	0.015	0.03	
	BLM41PG750SN1B			3500	2450			
	BLM41PG181SN1L	180±25%	180	*1	*1	0.02	0.04	
	BLM41PG181SN1B			3500	2100			
	BLM41PG471SN1L	470±25%	470	*1	*1	0.05	0.10	
	BLM41PG471SN1B			2000	1350			
	BLM41PG102SN1L	1000±25%	1000	*1	*1	0.09	0.18	
	BLM41PG102SN1B			1500	1000			

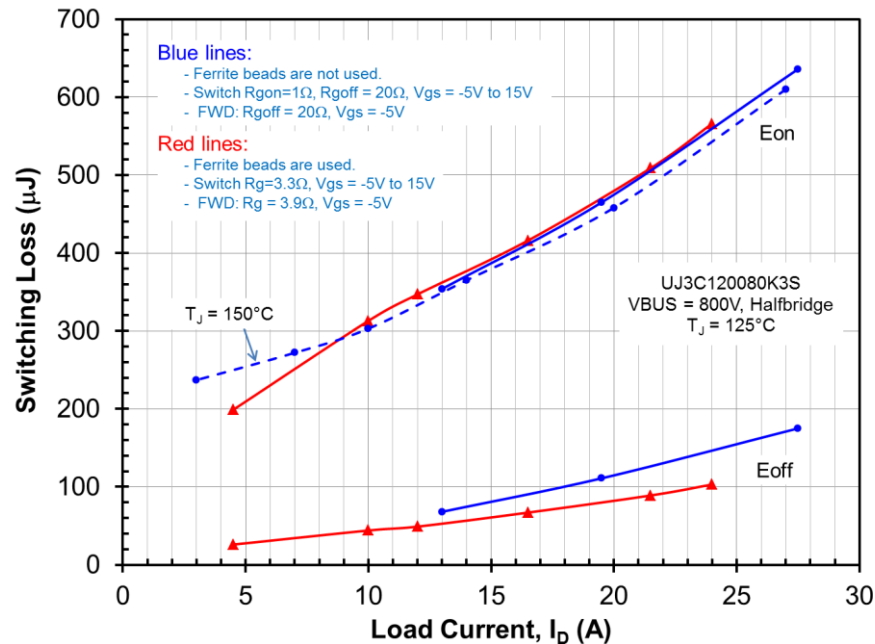• Operating Temperature: -55°C to +125°C • Storage Temperature: -55°C to +125°C



- Ferrite beads may be used to control gate ringing.
- Smaller R_{goff} values can be used with beads to reduce delay times, and reduce E_{off} .

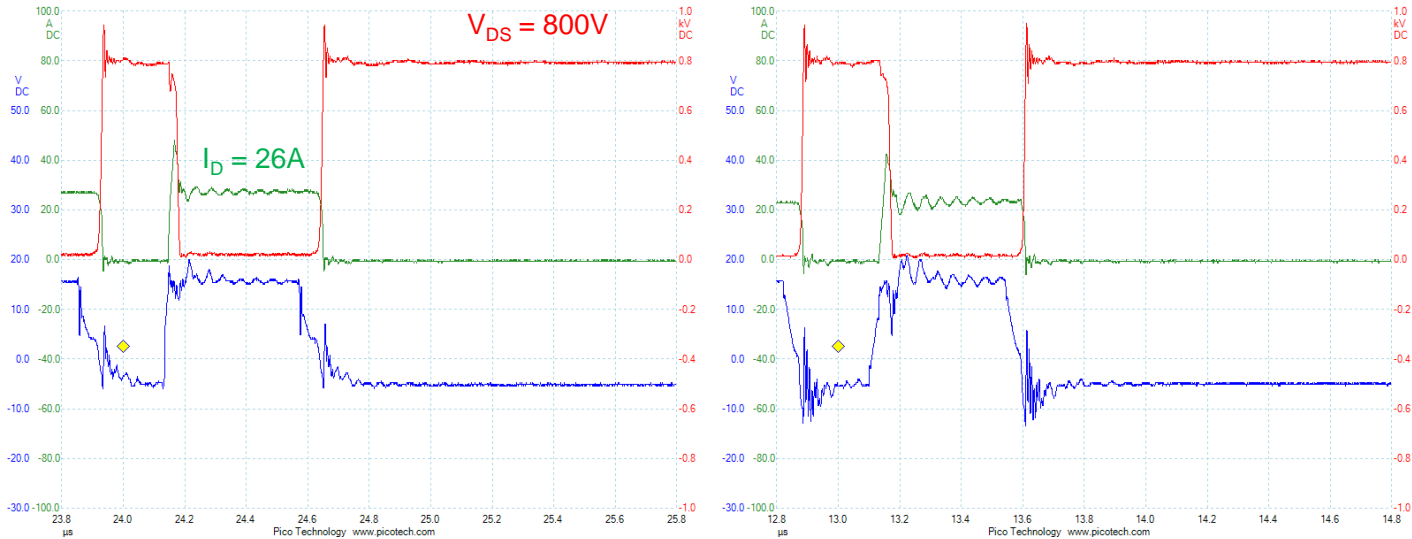Comparison of Switching Waveforms with and without using Ferrite Bead ($T_j = 125^\circ\text{C}$, 800V-26A)



Ferrite beads not used:

- Switch $R_{gon}=1\Omega$, $R_{goff} = 20\Omega$, $V_{gs} = -5\text{V}$ to 15V
- FWD: $R_{goff} = 20\Omega$, $V_{gs} = -5\text{V}$


Ferrite beads used:

- Switch $R_g=3.3\Omega$, $V_{gs} = -5\text{V}$ to 15V
- FWD: $R_g = 3.9\Omega$, $V_{gs} = -5\text{V}$


Using a ferrite bead, Turn-on peak current is lower with the bead since di/dt is reduced. Since lower R_g can be used with a ferrite bead, turn-off and turn-on delay times can be minimized.

Using Snubbers to manage switching waveforms

 - UnitedSiC FETs have low C_{OSS}
- Snubber capacitances needed are 1 to 3X of C_{OSS}
- Therefore, very small snubber capacitances are needed to control voltage overshoot and reduce current ringing
- The net loss impact is 1-5% of $E_{ON} + E_{OFF}$
- Small surface mount components are usable, since Snubber R_S loss is between 0.25W to 2W , depending on frequency (while switching 50A, 800V).







Hard Switching: Basic RC snubber

 

ZVS: RC snubber in series with de-coupling capacitor

Snubber Design for UF3C120040K3S

  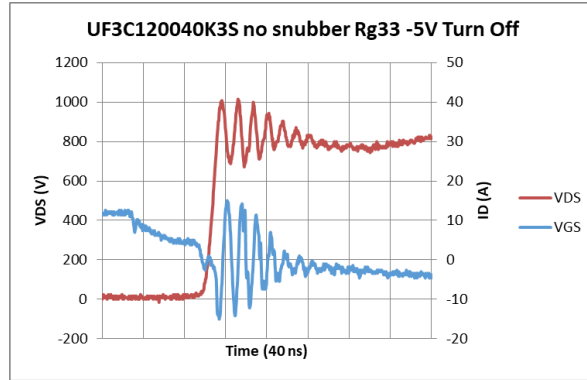 

- Cascode turn-off ringing may be reduced by high $R_{G,OFF}$ but this leads to long delay times
- Waveforms in the second row show how the V_{DS} and V_{GS} ringing are dramatically improved with a small snubber, switching the FETs at 50A, 800V.
- Snubber loss is <2.5% of total $E_{ON}+E_{OFF}$ at 10A and < 1.5% at 50A.


Measuring snubber resistor loss

UF3C120040K4S HALF_BRIDGE

VDS 800V, ID 50A, 125°C, VGS 20V/-5V,
Rgon 50Ω, Rgoff 33Ω,
Snubber Cs 115pF, snubber Rs 10Ω


CH1: Snubber Rs voltage (20V/div);
CH2: Drain current (20A/div);
CH3: VGS (10V/div);
CH4: VDS (200V/div).

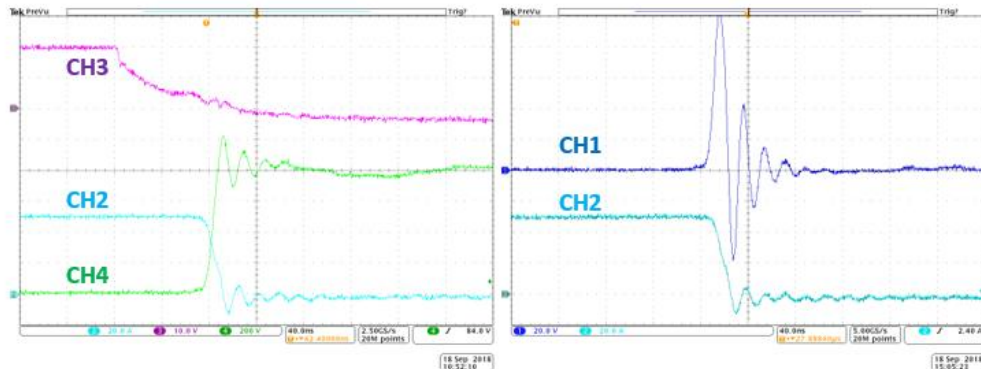- (a) Turn-off waveforms
- (b) Snubber Rs voltage at turn-off CH1
- (c) Turn-on waveforms
- (d) Snubber Rs voltage at turn-on CH1



(a)


(b)

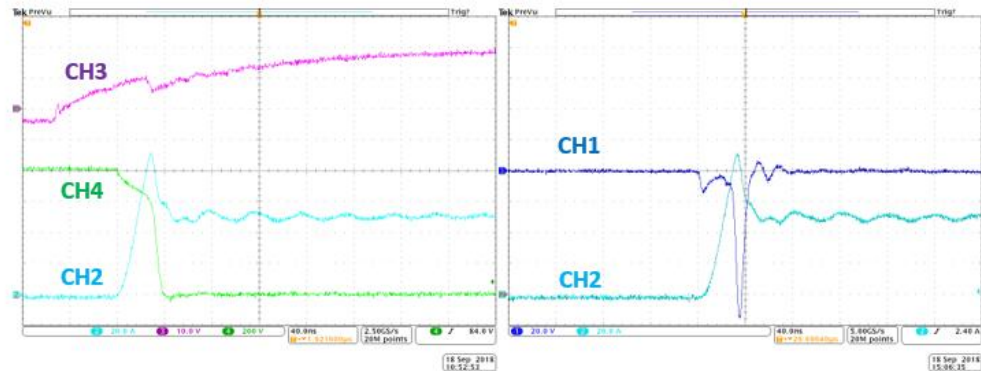

(c)

(d)

Snubber loss measured

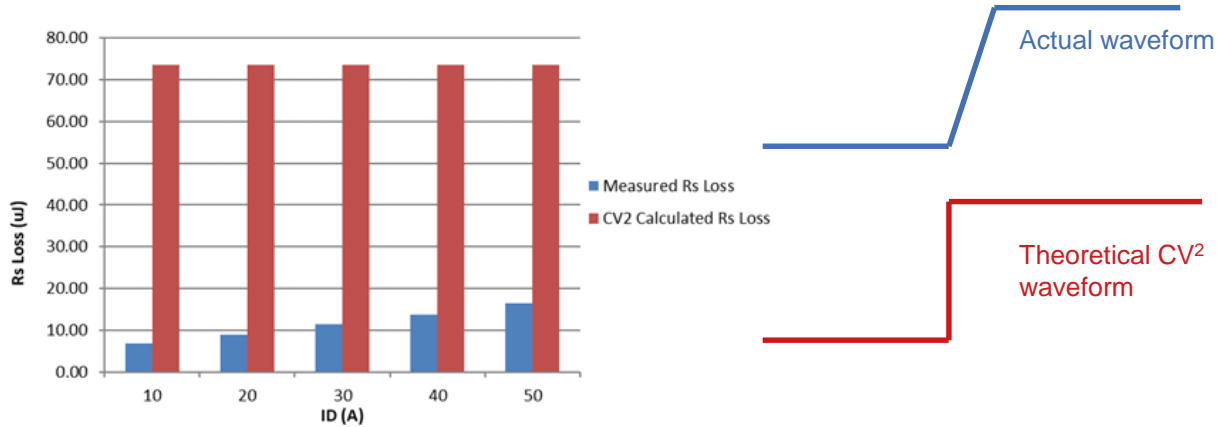

ID(A)	ESW(uJ)	ESNUB(uJ)	Ratio
10	494.8	6.86	1.39%
20	642.1	8.85	1.38%
30	811.1	11.39	1.40%
40	981.6	13.69	1.39%
50	1186.5	16.45	1.39%

10ohm, 115pF, 800V
UF3C120040K4S

UF3C120040K4S snubber Rs loss measurement vs. conventional CV^2 calculation.

This occurs because the CV^2 method assumes a constant charging voltage (infinite dV/dt), whereas practically, the device dV/dt regulates the maximum charging rate

Benefits of Kelvin packages

- Switch faster by overcoming common source inductance
- Cleaner gate waveforms, even with much faster di/dt




DFN8X8



D2PAK-7L



TO247-4L

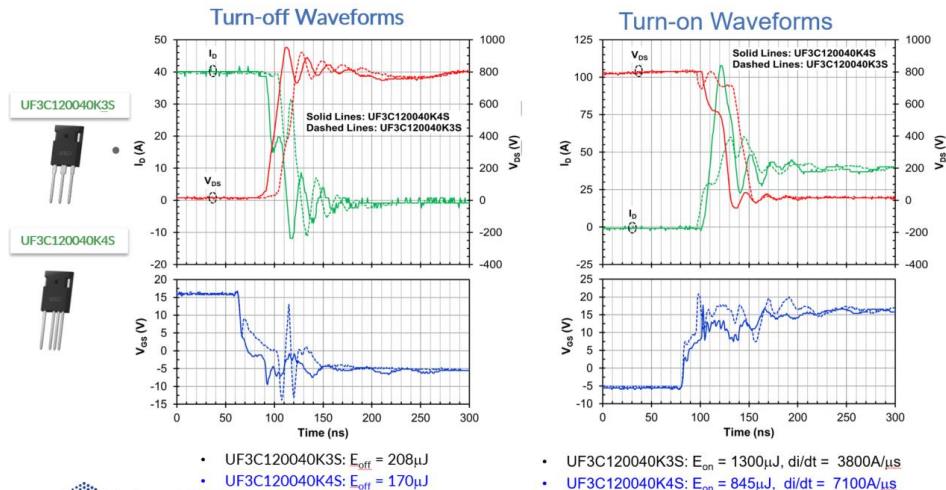


800V, 40A, Half-bridge, RT, $R_{gon} = 3\Omega$, $R_{goff} = 10\Omega$, FWD: $V_{GS} = -5\text{V}$, $R_g = 10\Omega$; $R_{SNUB} = 10\Omega$, $C_{SNUB} = 220\text{pF}$



Reduced Turn-on losses (E_{on})


Hard switched half-bridge

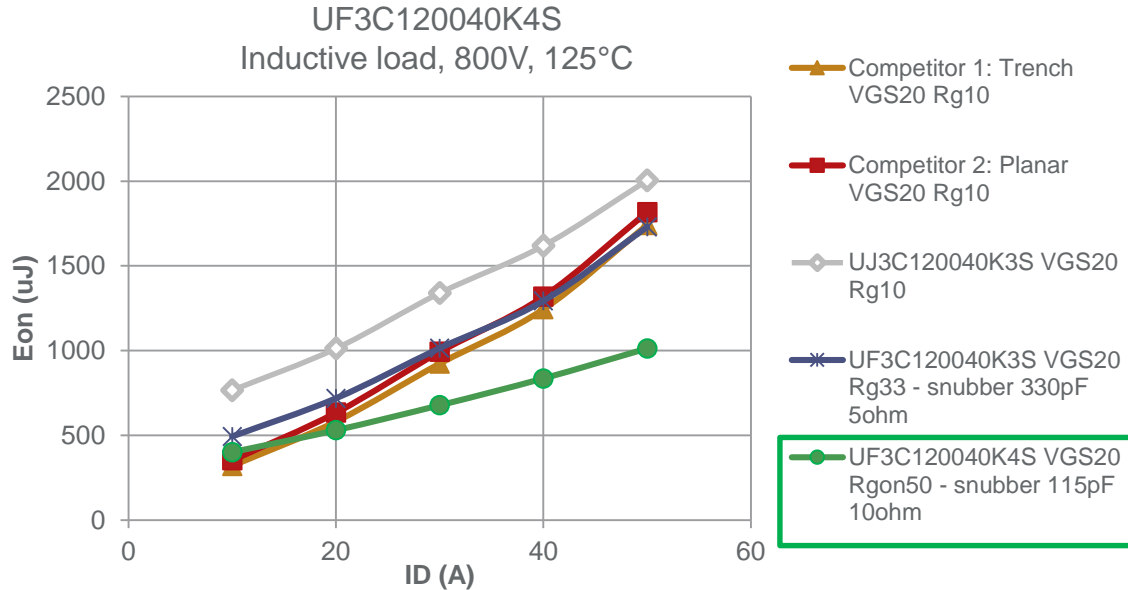

- *Dramatic improvement in E_{on} at higher current levels*
- *Snubber loss included*

Reduced Turn-off losses (E_{off})


Hard switched half-bridge

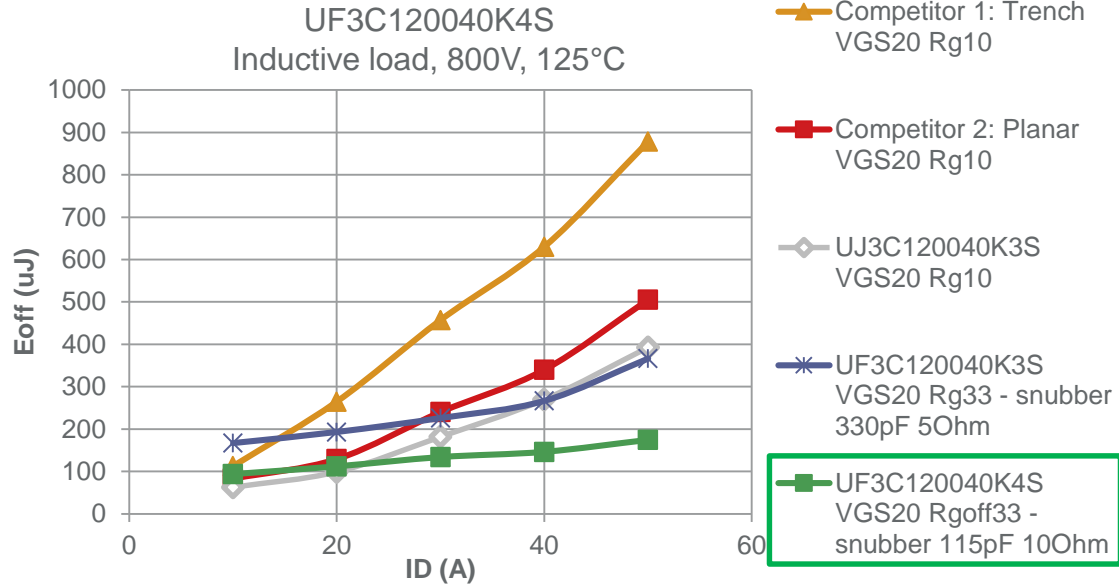

- *Very low E_{off} losses even at 50A*
- *Snubber loss included*

Excellent choice in soft switched circuits too

800V, 125C Soft Switching Effective Eoff

 

Effective turn-off loss \approx

$$E_{\text{off}} (\text{HS}) - (E_{\text{OSS}} + E_{\text{CS}})$$

New SiC FET User Guide

650V FETs

- ✓ Device selector by spec
- ✓ RC snubber guide
- ✓ End application device selection

Product Name	Package	V _{dsmax}	I _d (25C)		R _{thJC} (Typ)	R _{ds(on)} (25C)		R _{ds(on)} (175C)		Gate Drive voltage positive rail RGON				Gate Drive voltage negative rail RGOFF		RC snubber	R _{snub}	C _{snub}	E _{snub @ 10A}	E _{snub @ 30A}	C _{oss(er)}	Hard switched applications. Active rectifier, Totem Pole PFC, Full-bridge etc.			ZVS applications LLC		ZVS applications PSFB				
			A	A		C/W	mΩ	mΩ	10V	12V	15V	20V	0V	-5V	Ω							Ω	Ω	Ω	pF	μJ	μJ	pF	Upro 20kHz	20-100kHz	>100kHz
UJ3C065080T3S	TO220-3L	650	31	23	0.61	80	110	140	5	10	20	30	5	10	Optional	4.7	220							X			X		X		
UJ3C065080K3S	TO247-3L	650	31	23	0.61	80	110	140	5	10	20	30	5	10	Optional	4.7	220							X			X		X		
UJ3C065080B3	D2PAK-3L	650	25	18.2	1	80	110	140	5	10	20	30	5	10	Optional	4.7	220							X			X		X		
UF3C065080T3S	TO220-3L	650	31	23	0.61	80	110	140	5	10	20	30	10	20	Required	4.7	220								X						
UF3C065080K3S	TO247-3L	650	31	23	0.61	80	110	140	5	10	20	30	10	20	Required	4.7	220								X						
UF3C065080B3	D2PAK-3L	650	25	18.2	1	80	110	140	5	10	20	30	10	20	Required	4.7	220								X						
UF3C065080B7S	D2PAK-7L	650	TBD	TBD	TBD	80	110	140	15	20	30	50	5	10	Recommended	10	115							X	X		X	X	X		
UF3C065080K4S	TO247-4L	650	31	23	0.61	80	110	140	15	20	30	50	5	10	Recommended	10	115							X	X		X	X	X		
UF3C065040T3S	TO220-3L	650	54	40	0.35	42	58	78	5	10	20	30	10	20	Required	4.7	330								X			X	X		
UF3C065040K3S	TO247-3L	650	54	40	0.35	42	58	70	5	10	20	30	10	20	Required	4.7	330	16.0	23.0						X			X	X		
UF3C065040B3	D2PAK-3L	650	41	30	0.65	42	58	70	5	10	20	30	10	20	Required	4.7	330								X			X	X		
UF3SC065040B7S	D2PAK-7L	650	TBD	TBD	TBD	42	58	70	15	20	30	50	5	10	Recommended	10	110								X	X		X	X	X	
UF3C065040K4S	TO247-4L	650	54	40	0.35	42	58	70	15	20	30	50	5	10	Recommended	10	110								X	X		X	X	X	
UF3SC065040D8	DFN88	650	TBD	TBD	TBD	42	58	70	15	20	30	50	5	10	Recommended	10	110								X	X		X	X	X	
UJ3C065030T3S	TO220-3L	650	85	62	0.26	27	35	43	5	10	20	50	5	10	Optional	4.7	680							X			X		X		
UJ3C065030K3S	TO247-3L	650	85	62	0.26	27	35	43	5	10	20	50	5	10	Optional	4.7	680							X			X		X		
UJ3C065030B3	D2PAK-3L	650	66	47	0.48	27	35	43	5	10	20	50	5	10	Optional	4.7	680								X			X		X	
UF3C065030T3S	TO220-3L	650	85	62	0.26	30	39	48	5	10	20	30	10	20	Required	4.7	680								X			X	X		
UF3C065030K3S	TO247-3L	650	85	62	0.26	30	39	48	5	10	20	30	10	20	Required	4.7	680								X			X	X		
UF3C065030B3	D2PAK-3L	650	66	47	0.48	30	39	48	5	10	20	30	10	20	Required	4.7	680								X			X	X		
UF3SC065030B7S	D2PAK-7L	650	TBD	TBD	TBD	30	39	48	15	20	30	50	5	10	Recommended	10	220								X	X		X	X	X	
UF3C065030K4S	TO247-4L	650	85	62	0.26	30	39	48	15	20	30	50	5	10	Recommended	10	220								X	X		X	X	X	
UF3SC065030D8	DFN88	650	TBD	TBD	TBD	30	39	48	15	20	30	50	5	10	Recommended	10	220								X	X		X	X	X	

New SiC FET User Guide

1200V FETs

- ✓ Device selector by spec
- ✓ RC snubber guide
- ✓ End application device selection

Product Name	Package	Vdsmax	Id (25C)	Id (100C)	RthjC (Typ)	Rds(25C)	Rds(125C)	Rds(175C)	Gate Drive voltage positive rail RGON				Gate Drive voltage negative rail RGOFF		RC snubber	Rsnub	Csnub	Esnub @10A	Esnub @30A	Coss(er)	Hard switched applications. Active rectifier, Totem Pole PFC, Full-bridge etc.			ZVS applications LLC		ZVS applications PSFB									
									10V	12V	15V	20V	0V	-5V							Upto 20kHz	20-100kHz	>100kHz	50-150kHz	150-500kHz	20-50kHz	50-200kHz								
Units		V	A	A	C/W	mΩ	mΩ	mΩ	Ω	Ω	Ω	Ω	Ω	Ω		Ω	pF	uJ	uJ	pF															
UJ3C120150K3S	TO247-3L	1200	18.4	13.8	0.7	150	255	330	5	10	20	30	5	10	Optional	4.7	100			34	X			X			X								
UF3C120150K3S	TO247-3L	1200	18.4	13.8	0.7	150	255	330	5	10	20	30	10	20	Required	4.7	100																		
UF3C120150B7S	D2PAK-7L	1200	TBD	TBD	TBD	150	255	330	15	20	30	50	5	10	Recommended	10	47						X	X		X	X	X							
UF3C120150K4S	TO247-4L	1200	18.4	13.8	0.7	150	255	330	15	20	30	50	5	10	Recommended	10	47						X	X	X	X	X	X							
UJ3C120080K3S	TO247-3L	1200	33	24	0.45	80	136	172	5	10	20	30	5	10	Optional	4.7	150	5.0	8.0	59	X			X											
UF3C120080K3S	TO247-3L	1200	33	24	0.45	80	136	172	5	10	20	30	10	20	Required	4.7	150							X											
UF3C120080B7S	D2PAK-7L	1200	TBD	TBD	0.6	80	136	172	15	20	30	50	5	10	Recommended	10	68							X	X		X	X	X						
UF3C120080K4S	TO247-4L	1200	33	24	0.45	80	136	172	15	20	30	50	5	10	Recommended	10	68							X	X	X	X	X	X						
UJ3C120040K3S	TO247-3L	1200	65	47	0.27	35	56	73	5	10	20	30	5	10	Optional	4.7	330	14.7	21.6	112	X			X			X								
UF3C120040K3S	TO247-3L	1200	65	47	0.27	35	56	73	5	10	20	30	10	20	Required	4.7	330	16.1	23.5																
UFS3C120040B7S	D2PAK-7L	1200	TBD	TBD	TBD	35	56	73	15	20	30	50	5	10	Recommended	10	110							X	X		X	X	X						
UF3C120040K4S	TO247-4L	1200	65	47	0.27	35	56	73	15	20	30	50	5	10	Recommended	10	110	6.9	11.4						X	X	X	X							

Cs (pF)	Series	Part Number	Package	Rated V
47	COG	202R18N470JV4E	1206	2000V
68		C1206C680JGGAC7800	1206	2000V
100		202R18N101JV4E	1206	2000V
150		C1206C151JGGAC7800	1206	2000V
220		C1206C221JGGAC7800	1206	2000V
330		C1210C331JGGACTU	1210	2000V
680		C1808C681JGGAC7800	1808	2000V

"COG" ceramic capacitors are most stable.

Rs (Ω)	Power Rating (W)	Part Number	Package
4.7	0.25	KTR18EZPF4R70	1206
	0.5	SR1206FR-7W4R7L	1206
	1	CRCW20104R70JNEFHP	2010
	1.5	CRCW25124R70JNEGHP	2512
10	0.25	KTR18EZPF10R0	1206
	0.5	SR1206FR-7W10RL	1206
	1	CRCW201010R0JNEFHP	2010
	1.5	CRCW251210R0JNEGHP	2512

For "KTR18" resistor is rated at 500V and the overload voltage is 1000V.

For "SR1206" resistor is rated at 200V, the overload voltage is 400V, the dielectric withstanding voltage is 500V.




URL - <https://unitedsic.com/cascodes/>


Paralleling discrete devices for higher power

GENERAL GUIDELINES FOR PCB LAYOUT

 - Symmetry
- Minimum PCB stray inductances
- Separate gate resistor
- Minimize capacitive coupling between gate and drain of each transistor.



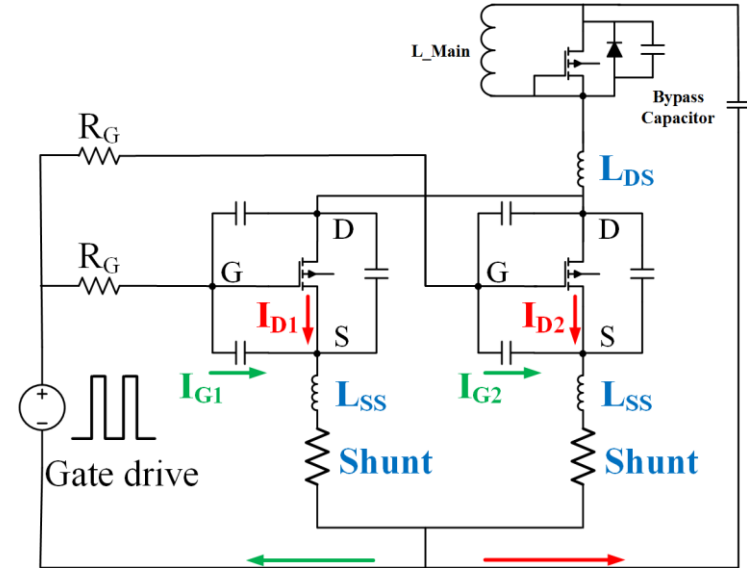
R_{ds} positive temperature coefficient
aids current sharing




L_{DS} : main loop stray inductance
 L_{SS} : common source inductance

Paralleling discrete devices for higher power

 
Parallel turn on with same V_{th} @ 25 °C,
 $R_{gon} = 10 \text{ Ohm}$, $V_{ds} = 850 \text{ V}$, $I_s = 36 \text{ A}$



 
Parallel turn on with different V_{th}
@ 25 °C, $R_{gon} = 10 \text{ Ohm}$, $V_{ds} = 850 \text{ V}$, $I_D = 36 \text{ A}$



 
Turn on with same V_{th} , #3 @ 65 °C, #5 @ 25 °C,
 $R_{gon} = 10 \text{ Ohm}$, $V_{ds} = 850 \text{ V}$, $I_s = 36 \text{ A}$



 
Parallel turn off with same V_{th} @ 25 °C,
 $R_{goff} = 32 \text{ Ohm}$, $V_{ds} = 850 \text{ V}$, $I_s = 36 \text{ A}$



 Parallel turn off with different V_{th}
@ 25 °C, $R_{goff} = 32 \text{ Ohm}$, $V_{ds} = 850 \text{ V}$, $I_s = 36 \text{ A}$



 Turn off with same V_{th} , #3 @ 65 °C, #5 @ 25 °C,
 $R_{goff} = 32 \text{ Ohm}$, $V_{ds} = 850 \text{ V}$, $I_s = 36 \text{ A}$



UnitedSiC FET paralleling is tolerant of typical parametric mismatches and temperature differentials





V_{th} mismatch

T_j mismatch of 40C

Scalable SiC Cascode Power Blocks

 
 
Conventional Method:
Single external gate driver and capacitor at module level => All circuit legs switch through common parasitic inductance.



Preferred Method:
Local bus capacitance and gate drive buffer for each circuit leg => High frequency switching contained within each converter leg.




Layout of 8 Parallel Legs

  


Power loop showing the Bottom of the PCB, the central "bus bar", and the gate drive loops on the Top layer

Scalable SiC Cascode Power Blocks

 

 Power blocks have been built for half-bridges and TNPC units with upto 8X units in parallel



Switching of a power block with 4X HS and 4X LS SiC FETs





United **Sic**

Simply More Efficient


APPENDIX

How the cascode FET works

 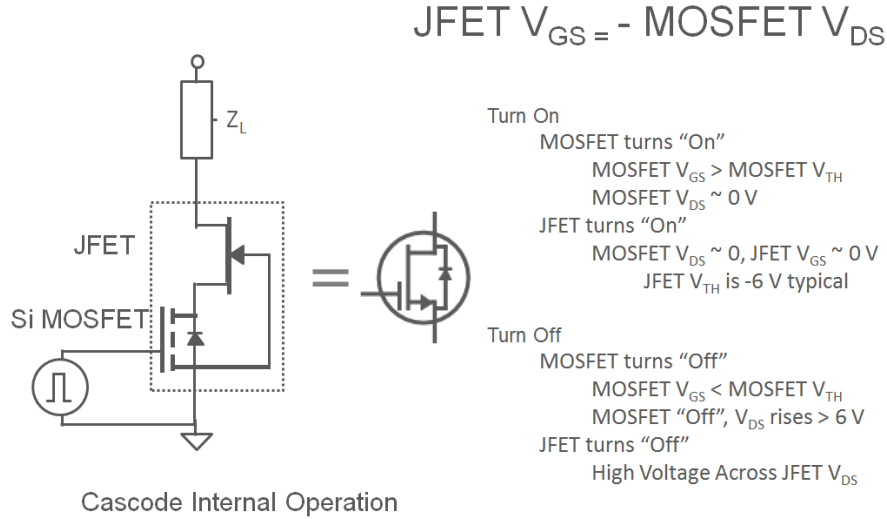

Easy to Cascode JFET Design

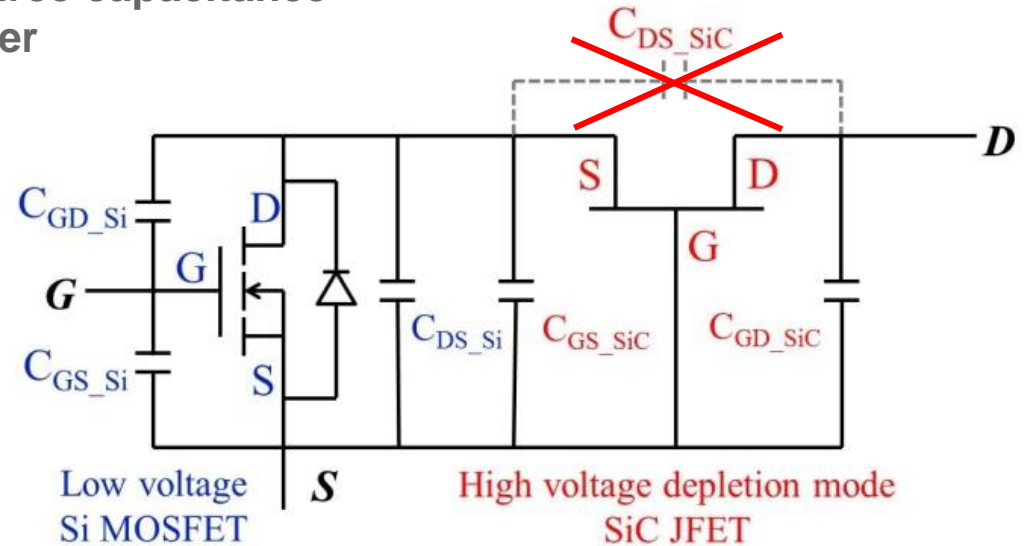- UnitedSiC JFET has zero drain-source capacitance
- No drain-source-gate voltage divider
- Good for ZVS operation
- Stable



Ref: X. Huang, W. Du, F.C. Lee, Q. Li and Z. Liu, "Avoiding Divergent Oscillation of a Cascode GaN Device Under High-Current Turn-Off Condition", IEEE Trans. Power Electron., 2017

Body Diode V_F : UnitedSiC FET vs SiC MOSFET

Low V_F & Q_{rr}
eliminates need
for separate
anti-parallel
diode

 


Figure 10 3rd quadrant characteristics
at $T_J = 25^\circ\text{C}$


 
 





Figure 14. 3rd Quadrant Characteristic at 25°C

What controls switching speeds




- Turn-on di/dt can be slowed by MOSFET R_{gon} in a TO247-3L, where L_s de-biases the $V_{gs(MOS)}$. So higher V_{gs} values can speed up di/dt .
- The upper limit to the di/dt is set by the fact that the JFET V_{th} is fixed, and the JFET experiences a $V_{GS(JFET)} = -V_{DS(MOS)}$ that is fixed. The internal inductance and the $R_{GJFET} * (C_{gsJ} + C_{oss(MOS)})$ sets this maximum di/dt .
- Once the MOSFET has turned off enough to pinch-off the JFET, dV/dt is largely regulated by the $C_{gdJ} * R_{GJFET}$. However, slowing the MOSFET drain node using an external R_{goff} can influence the turn-off rate, essentially slowing the gate voltage applied to the JFET at turn-off.

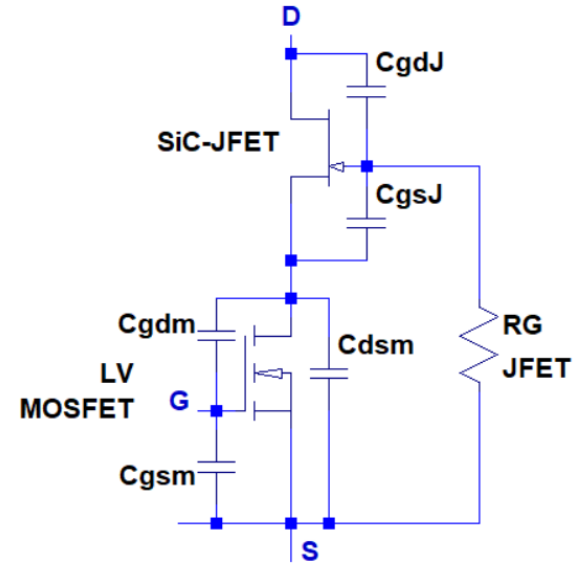

   Measured Turn-on Energy Loss, di/dt and dv/dt with 600V Inductive Load. FWD: UJC1206K




   Measured Turn-off Energy Loss, di/dt and dv/dt with 600V Inductive Load Condition. FWD: UJC1206K




Comparing G2, G3 cascodes and SiC MOSFETs in half-bridge

 
UJC1210K, 12V/-5V
 $R_{gon} = 2.3 \Omega$, $R_{goff} = 10 \Omega$, $E_{on} = 406 \mu\text{J}$
 $di/dt = 1.28 \text{ A/ns}$, $dv/dt = 69 \text{ V/ns}$



 
UJ3C120080K3S, 15V/-5V
 $R_{gon} = 1 \Omega$, $R_{goff} = 20 \Omega$, $E_{on} = 392 \mu\text{J}$
 $di/dt = 2.78 \text{ A/ns}$, $dv/dt = 78 \text{ V/ns}$




C2M080120D, 18V/-5V
 $R_{gon} = 5 \Omega$, $R_{goff} = 5 \Omega$, $E_{on} = 446 \mu\text{J}$
 $di/dt = 2.1 \text{ A/ns}$, $dv/dt = 71 \text{ V/ns}$

 

 
UJC1210K
 $R_{gon} = 2.3 \Omega$, $R_{goff} = 10 \Omega$, $E_{off} = 101 \mu\text{J}$
 $di/dt = 4.2 \text{ A/ns}$, $dv/dt = 86 \text{ V/ns}$







 
UJ3C120080K3S
 $R_{gon} = 1 \Omega$, $R_{goff} = 20 \Omega$, $E_{on} = 107 \mu\text{J}$
 $di/dt = 3.7 \text{ A/ns}$, $dv/dt = 85 \text{ V/ns}$







 
C2M080120D
 $R_{gon} = 5 \Omega$, $R_{goff} = 5 \Omega$, $E_{off} = 115 \mu\text{J}$
 $di/dt = 2.3 \text{ A/ns}$, $dv/dt = 60 \text{ V/ns}$



     UJ3C120080K3S Half-bridge Vgs drive +15V/-5V Rgon=1ohm, Rgoff=20ohm, 125C



     UJ3C120080K3S Half-bridge Vgs drive +15V/-5V Rgon=2.3ohm, Rgoff=8ohm, 125C



UJ3C switching characteristics

80m, 1200V

 


Figure 18 Clamped inductive switching energy vs. drain current at $T_J = 150^\circ\text{C}$

 


Figure 20 Clamped inductive switching turn-off energy vs. R_{G,EXT_OFF}

 


Figure 21 Clamped inductive switching energy vs. junction temperature at $I_D = 20\text{A}$

UJ3C switching characteristics

30m, 650V

 


Figure 18 Clamped inductive switching energy vs. drain current at $T_J = 150^\circ\text{C}$

 


Figure 20 Clamped inductive switching turn-off energy vs. $R_{\text{G,EXT_OFF}}$



 
 


Figure 21 Clamped inductive switching energy vs. junction temperature at $I_D = 50\text{A}$

 Measured Qrr of UJ3C120040K3S vs UF3C120040K4S





 Minimum Qrr in a cascode is Qc, the integrated Coss charge





UF3C120080K4S

Half-Bridge Switching Energies

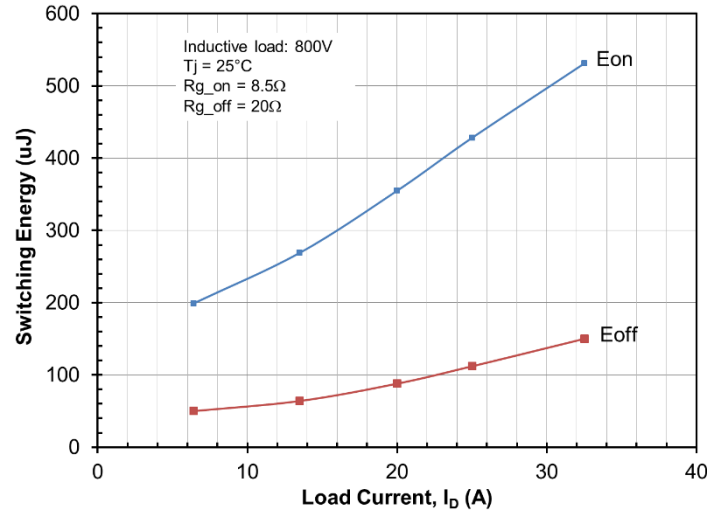 

UF3C120080K4S Switching Waveforms

  800V, $T_j = 25^\circ\text{C}$, $V_{gs} = -5\text{V}/+12\text{V}$



$R_{g_on} = 1\Omega$
 $R_{g_off} = 47\Omega$
Turn-on $di/dt = 8563\text{A}/\mu\text{s}$

$R_{g_on} = 21\Omega$
 $R_{g_off} = 47\Omega$
Turn-on $di/dt = 1995\text{A}/\mu\text{s}$








ZVS circuits LLC, PSFB

- Since turn-on is no longer critical, it should generally be possible to use a single R_{goff} .
- Depending on current 5-20ohm works well
- Sufficient to limit gate drive to 0-12V – no benefit with higher V_{gs} , no benefit with negative gate drive
- A bead can still be used if currents are high, or if a low R_{goff} is required to minimize delay time at high frequencies


650V cascode – Totem Pole PFC

     Uniquely qualified for use in CCM Totem Pole PFC due to excellent Body Diode



Snubber Design for UF3C120080K4S series


Test Conditions

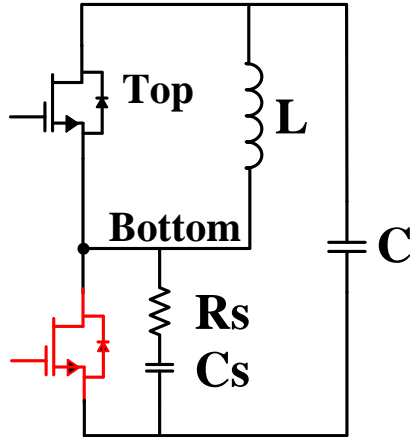

- Top switch is the freewheeling device
- VDS, ID are measured for the bottom switch
- VGS: +15V turn on, -5V turn off
- Rgon 10Ω, Rgoff 10Ω
- VDS 800V
- ID: 25A
- Temperature: 120°C both top & bottom switch
- Snubber: 10Ω, 220pF
- When adding a snubber, switching loss includes both device and snubber loss.
- DUT: UF3C120080K4S

Snubber Design for UF3C120080K4S series

No Snubber, 25A, 800V, 120°C

 


- The measurement on the left shows more VDS ringing at turn-off transient than turn-on.
- Therefore the snubber should be placed on the bottom switch.

Time: 400ns/div ID: 20A/div VGS: 10V/div VDS:
200V/div

30 Apr 2018
14:21:53

Snubber Design for UF3C120080K4S series

Guideline for snubber design

 

The Cadd is a ceramic capacitor rated at 220pF. At 800V the ceramic capacitor capacitance is around 150pF which is also close to $C_s = 148\text{pF}$. Hence, C_s is the same as Cadd.

The VDS ringing frequency is **100MHz** (f_0).
Adding a Cadd (220pF) reduces frequency to 42MHz (f_1).
Therefore the circuit stray capacitance CLK is 47.1pF.

$$CLK = \frac{C_{add}}{(f_0/f_1)^2 - 1}$$

Therefore the circuit leakage inductance LLK is 54nH.

$$LLK = \frac{1}{(2\pi f_0)^2 CLK}$$

If damping factor $\zeta = 1.6$, **$R_s = 10\Omega$**

$$R_s = \frac{1}{2\zeta} \sqrt{\frac{LLK}{CLK}}$$


If cutoff frequency $f_c = 68.5\text{MHz}$, **$C_s = 220\text{pF}$** .

$$C_s = \frac{1}{2\pi R_s f_c}$$


Snubber Design for UF3C120080K4S series

Trade off's using a snubber

 No Snubber
 $E_{on} = 363\mu\text{J}$, $E_{off} = 64\mu\text{J}$



 With Snubber
 $E_{on}^* = 371\mu\text{J}$, $E_{off}^* = 147\mu\text{J}$



Time: 20ns/div ID: 10A/div VDS: 200V/div

The E_{on}^* , E_{off}^* with snubber are the total loss of device and snubber.

- Cascade turn-off ringing may be reduced by high R_{goff} but this leads to long delay times
- Quick and easy solution to use fast SiC devices in existing designs without causing excessive ringing


Customer Reference: Micropower

- Phase shifted Full bridge
 - Need for an excellent body diode
- 10kW battery charger
- Technological partnership
- RESULTS:
 - 30% higher output power with UnitedSiC FET in same dimensions
 - Easy to replace Si-FET replacement using standard gate drive
 - 1.5% higher efficiency

MICROPOWER GROUP™
POWERFUL SOLUTIONS PARTNER




UnitedSiC FET advantage in PSFB

 

- Previous technologies include IGBT, super-junction MOSFET, and SiC MOSFET
- IGBTs have very high turn-off switching power loss, slow-switching reverse diode
- Super-junction MOSFETs have larger chip size, slow-switching reverse diode
- SiC MOSFET has larger chip size, asymmetric gate drive (-5 to 18 V typically)
- UnitedSiC FET is the best performing PSFB switch

Battery Charger topology

 
A non controlled traditional battery charger (rectifier) provides a simple direct **AC/DC conversion**




Disadvantages of this solution are:

- Low efficiency
- Large physical size
- Long charge times
- Charge depends on changes in the mains supply (with overcharge danger in the final charge phase)

Block Scheme

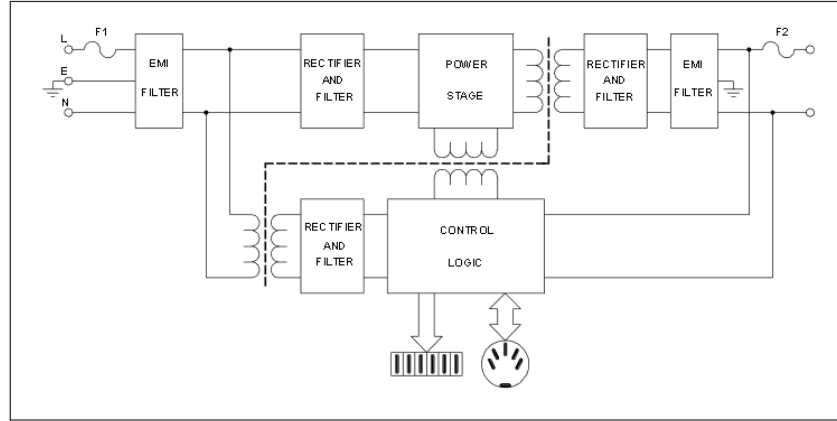

 In modern battery chargers these disadvantages are solved with an **indirect AC/DC conversion**, by passing through an intermediate DC/DC conversion.



This is the usual method of operation for the SMPS (Switching Mode Power Supply) at high power. This solution gives a good performance for minimum costs and physical dimensions using switches more faster and powerful (modern technology).

The main advantages of this solution are:

- High efficiency
- Reduced dimensions
- Short charge times
- Charge independent from the changes of the mains supply
- Electronic control that provides the desired charge curve